



The right technology for solar converters

Introduction

Following a short overview of types of solar power systems and converters, this application note introduces a fully working, grid-connected solar inverter prototype suitable for rooftop applications. This solar inverter has been equipped with STMicroelectronics' MDmesh™ and silicon carbide (SiC) devices to allow evaluation of these products in "green" technologies.

Thanks to ST's newest technologies (MDmesh™ V and SiC) and a new converter philosophy, a 650 V fast power MOSFET can be used to boost performance and reduce the size of the converter. A stage-by-stage explanation is presented here, as well as the topologies adopted, and a detailed analysis of the front-end stage of the inverter is discussed. The BOOST stage is used as a case study to validate the performance of the new power MOSFETs and diodes.

Everyone is thinking "green" these days. Adding to the new green conscience are the increasing costs of fossil and nuclear fuels, prompting the market to turn to creative technologies that use renewable resources to produce energy. Energy produced from renewable resources are becoming an important contribution to the world's total energy demand and will increase in the next decades. Solar photovoltaic technology represents one of the most promising energy resources, due to its low environmental impact and high reliability. Every photovoltaic (PV) system consists of a module array and an inverter. The inverter module is mandatory on all grid-connected applications, in order to amplify the low DC voltage generated by the module to the higher AC level required by the grid. If several modules are connected in series it might not be necessary to include amplification, but in any case a maximum power point tracking (MPPT) function is required.

This prototype has a wide operating input voltage range (from 200 V to 400 V), and 3 kW of maximum power output, since it is intended for rooftop applications. Total efficiency must be at least 97%, and an MPPT function is implemented in order to enable panels to work at their highest efficiency. In fact, the PV module (or modules, if connected in series) changes its maximum power point continually during normal operation due to the variances in solar radiation caused by shade or weather.

Contents

1 Solar power systems and inverters 4

2 Grid connected inverter 5

3 Measurements on the BOOST stage 9

4 SiC technology vs. silicon 14

5 Conclusion 15

6 Revision history 16



List of figures

Figure 1.	Block diagram	5
Figure 2.	BOOST stage	6
Figure 3.	Power transformer and rectification stage	6
Figure 4.	BUCK current generator stage	7
Figure 5.	100 Hz bridge sync rectifier stage	7
Figure 6.	Efficiency vs. power output on BOOST stage @ $R_g=8.2\ \Omega$ and $di/dt = 1400\ W$	9
Figure 7.	Typical waveform during normal operation on BOOST stage @ $P_{OUT} = 1300\ W$	10
Figure 8.	Turn-on waveform on BOOST stage @ $P_{OUT} = 1700\ W$, $V_{IN} = 200\ V$	11
Figure 9.	di/dt vs. gate resistance value @ total parasitic inductance of 110 nH on the power loop	12
Figure 10.	I_{peak} vs. di/dt @ $P_{OUT} = 1900\ W$	13
Figure 11.	Silicon vs. SiC diode comparison @ $I_F = 5\ A$, $di/dt = 840\ A/\mu s$	14

1 Solar power systems and inverters

There are a wide variety of topologies employed in the design of converters for solar power systems, but they can be separated into two main classifications:

- Grid connected:
 - These are usually isolated residential PV panels or collections of panels, called “farms”, connected to a central power facility maintained by a private or public company. Therefore, the energy produced from these photovoltaic modules during the day can be used immediately on the main grid. These systems do not require storage batteries or any backup system to store the energy, because the main grid continues to supply energy at night or in the absence of sunlight.
- Standalone:
 - These are used on systems typically far from a municipal or public power grid. These systems use a battery, or bank of batteries, to store the energy produced during the day by the panels, in order to provide a supply of energy at night or when solar irradiation is low. Grid connected inverters are generally more complex than the standalone because they must synchronize with the grid sinusoid and supply the current within the same phase. However, the first stages of design are quite the same on both types of inverters. Traditionally, solar systems used to implement a single, shared inverter for all panels. This is called a “centralized” system. The trend today is toward a “string inverter” system, in which each panel is equipped with its own low power and high performance inverter. Each of the inverters mentioned previously can be designed following two different approaches with respect to frequency operation. If a low frequency approach is adopted (typically 100 Hz), very slow devices can be used. However, in this case very heavy transformers and bulk capacitors are necessary. Generally, newer designs adopt high frequency operation in order to minimize inverter dimensions and weight and to maximize performance. It is worth mentioning that in our example we have performed the tests on a 3 kW grid-connected inverter, but the same benefits can be obtained in each of the types of inverters previously mentioned.

2 Grid connected inverter

A PV inverter must perform three main functions in order to feed energy from a PV array into the utility grid:

1. Shape the current into a sinusoidal waveform
2. Invert the current into an AC current
3. Boost the PV array voltage if it is lower than the grid voltage

The way these functions are sequenced within an inverter design determines the choice of semiconductor and passive components, and consequently their losses, sizes and prices. In order to validate new technologies, a solar inverter prototype was developed and equipped with ST MDmesh™ and SiC devices. The block diagram is shown in [Figure 1](#), and block-by-block details are shown in [Figures 2, 3, 4 and 5](#).

Note: The new approach and topologies of each stage allow the use of a 650 V power MDmesh™.

Figure 1. Block diagram

 


Figure 2. BOOST stage

 


Figure 3. Power transformer and rectification stage

 


Figure 4. BUCK current generator stage


 


Figure 5. 100 Hz bridge sync rectifier stage

 

The first stage, called the “BOOST” stage, is common to most solar inverters and power factor correction (PFC) converters. A converter used as a front-end between PV panels and inverter, amplifies the panel voltage into a DC BUS from 400 V to 500 V for 3 kW output power. The BUS voltage should be lower than 450 V in order to permit the use of 450 V capacitors, typically less expensive than 500 V capacitors. In order to limit the peak value of the current on both the power MOSFET and the diode, this BOOST stage operates in

continuous current mode, so the power MOSFET is turned on during the recovery time of the diode. The BOOST is driven from a microcontroller in order to implement the MPPT. Some inverter modules adopt a push-pull topology instead of the boost topology, to elevate the panel solar voltage and achieve galvanic insulation. In this case, more expensive devices sized for two times the input voltage must be used. If the BUS voltage is 500 V, the devices must be able to manage at least 1000 V, so 1200 V devices are needed. IGBTs are commonly used for this voltage range, due to acceptable conduction loss levels. Unfortunately, IGBTs are not fast devices and they must be used at relatively low frequencies in order to minimize switching losses. The boost topology permits the use of more efficient 600-650 V power MOSFET devices, and pushes up the switching frequency. A higher frequency means smaller and cheaper inductor and bulk capacitors.

The second stage is a “power transformer” stage, as shown in [Figure 3](#). This is used to provide galvanic insulation between the panels and the grid. This block is not mandatory in some countries but is generally used for safety reasons. Its frequency of operation is about 100 kHz in order to minimize transformer size. The power MOSFETs are connected in a typical bridge configuration, and the devices work on a modified zero-voltage switching (ZVS) modulation to minimize the switching losses. The bus voltage is 450 V (typ).

The “high performance bridge rectifier” stage is used to rectify the alternating voltage coming from the “power transformer.” It is composed of four SiC diodes connected in a Graetz bridge, as shown on the right side of [Figure 3](#). These diodes are able to work at very high di/dt, typically greater than 1000 A/μs. The operating frequency is the same as that of the “power transformer” stage, about 100 kHz.

The “current generator” stage is used to provide and regulate the power generated from solar panels onto the grid. It consists of a typical buck topology composed of an MDmesh™ V power MOSFET and a SiC diode, as shown in [Figure 4](#). The operating frequency is about 100 kHz, and the drive signal is modulated in order to follow the 100 Hz of the grid.

The last stage is the “sync bridge rectifier.” This is a simple Graetz bridge used to rectify the grid and allow the “current generator” to introduce power to the grid during the full sinusoid. It is composed of four power MOSFETs specially driven and used as synchronous rectifiers (see [Figure 5](#)). Please note that this stage can be realized with simple diodes, but for efficiency issues we use a MOSFET as a synchronous rectifier, grid-commutated at twice the grid frequency. Grid-commutated operation is possible because the input current to the stage is modulated to the rectified sinusoidal by the “current generator” stage.


Thanks to this solution, a single switch current generator can be adopted using the STW42N65M5 or STW77N65M5 650 V power MOSFETs. Currently, most solutions adopt a half-bridge current generator topology instead of a single switch. These solutions are able to follow the grid voltage on a full sinusoid, but 600-650 V power MOSFETs cannot be used due to their low breakdown voltage. In fact, in this case the power MOSFETs must be able to manage at least 750 V on the bus voltage (double the maximum peak-to-peak grid voltage ± 373 V). If a full-bridge inverter topology is used to design a current generator (to unfold the power to grid, synchronized to the sine wave), PWM modulation must be used. Both fast switches and diodes must be used in order to increase efficiency. IGBT devices with a paralleled discrete fast diode are generally used, due to better performance with respect to the power MOSFET solution. IGBTs are preferred based on the higher performance of the discrete fast diodes with respect to a power MOSFET internal body diode. Due to the circuit solutions adopted on this proposed new inverter design, 650 V MDmesh™ V MOSFETs can be safely used (STW42N65M5 or STW77N65M5). Using MDmesh™ combined with 600 V SiC diodes (STPSC1006) allows us to increase the frequency of operation and work at high di/dt, from 800 A/μs to 2 kA/μs, and more. The capability to operate at a high frequency translates into being able to use the smallest (and magnetic) transformer, and even smaller capacitors.

3 Measurements on the BOOST stage

Although MDmesh™ power MOSFETs and SiC diodes are used on every stage of the inverter, the following results derive from the inverter front-end stage called the BOOST stage. This stage is used as a case study to validate the performance of the fastest power MOSFETs and diodes available on the market. The basic BOOST configuration is very similar to other applications like a traditional single switch PFC, as shown in [Figure 2](#), but in this case, the input voltage is continuous rather than pulsed. Efficiency is measured in the worst conditions, which means at the lowest input voltage, so that at full load the input current is the highest possible. Note that higher-speed commutation leads to higher efficiency, but at the same time spike voltage and current stimulus on the main switch are higher also. Therefore finding a good trade-off is recommended. In any case, a 650 V breakdown voltage keeps the MDmesh™ V within a safe working zone. An STW42N65M5 and an STPSC1006 are used for this stage. [Figure 6](#) shows the efficiency versus output power, at $V_{DC\,IN} = 200\text{ V}$ and gate resistance $R_g = 8.2\ \Omega$

With $8.2\ \Omega$ we achieved a di/dt of $1400\text{ A}/\mu\text{s}$ during turn-on, which provides good noise immunity and low EMI irradiation.

Figure 6. Efficiency vs. power output on BOOST stage @ $R_g = 8.2\ \Omega$ and $di/dt = 1400\text{ W}$

 

[Figure 7](#) shows the BOOST signals during normal operation at $V_{IN} = 200\text{ V}$, $V_{OUT} = 450\text{ V}$, and $P_{OUT} = 1300\text{ W}$. [Figure 8](#) shows the detailed BOOST signals during turn-on at $V_{IN} = 200\text{ V}$, $V_{OUT} = 450\text{ V}$, and $P_{OUT} = 1700\text{ W}$. Please note the peak current on the trace in black

(about 22 A). This is due to the SiC capacitance discharge at high $di/dt = 1400 \text{ A}/\mu\text{s}$. The step on the drain voltage (trace in red) is due to parasitic inductance of the board. The violet trace represents the energy losses during turn-on. Turn-off is performed with a signal diode connected in parallel to the 8.2Ω resistor, so for turn-off the equivalent R_{GATE} is zero, in order to obtain the fastest commutation speed. All measurements have been performed on a grid-connected 3 kW solar inverter prototype, totally equipped with both MDmesh™ and SiC devices.

Figure 7. Typical waveform during normal operation on BOOST stage @ $P_{\text{OUT}} = 1300 \text{ W}$

 


 
Figure 8. Turn-on waveform on BOOST stage @ $P_{OUT} = 1700\text{ W}$, $V_{IN} = 200\text{ V}$ 

Table 1 summarizes the results of the measurements performed by varying the R_g gate resistor value. Please note that we use a gate resistor just for turn-on. For turn-off, a simple diode is used, connected in parallel to the gate resistor. It should be highlighted that lower R_g values lead to improved efficiency over the entire power output scale. But at the same time this means higher spike voltage and current during commutation. By using a lower gate resistor you get better efficiency, but also higher peak recovery current and higher di/dt . This could be a problem for EMI irradiation and reliability, so an $8.2\ \Omega$ and 1400 A di/dt should be a good compromise.

Table 1. di/dt and I_{peak} vs. R_{gate} during turn-on @ $P_{OUT} = 2000\text{ W}$, $V_{IN} = 200\text{ V}$

$R_g\ (\Omega)$	$I_{ON}\ di/dt\ (A/\mu s)$	$I_{ONpeak}\ (A)$	Efficiency @ $P_{OUT} = 2\text{ kW}\ (\%)$
3.9	2200	26.6	98.52
5.6	2000	24.7	98.40
8.2	1400	20.6	98.27
15	800	17.4	98.14

Although designers strive to keep all board parasitic influences to a minimum, they cannot be eliminated completely due to the physical limitations related to component dimensions. The copper tracks on the board must be as short as possible, but in any case must be long

enough to connect every component. So, assuming that parasitic impedances are still present, even if very small, they present problems in addition to an increase in operating frequency. Parasitic effects lead to:

- losses during commutation
- spike voltage
- EMI irradiation
- reliability problems leading to failures in extreme cases

For this reason, designers tend to optimize the layout and limit the very fast commutations by increasing the gate resistor. According to our tests, the I_{ON} di/dt can be controlled by fine tuning the R_g gate resistance used to drive the power MOSFET during turn-on (STW42N65M5). [Figure 9](#) shows the di/dt vs. gate resistance value by using a board with about 110 nH of total parasitic inductances (about 12 cm of total parasitic inductance on the power ring loop). [Figure 10](#) shows the peak current obtained by using a different gate resistance value, with about 120 nH of total parasitic inductances. These graphs can be useful to obtain a rough estimate of the gate resistor dimensions, with the di/dt function or maximum peak current you wish to obtain, considering that di/dt commutation speed depends on many parameters (such as power MOSFET + diode and the board). It is recommended to test the results with the selected power MOSFET in every board, in order to achieve the best performance. It should be noted that MDmesh™ power MOSFETs and SiC diodes are able to work with very high di/dt, but in any case in a project it is preferable to limit the commutation speed in order to keep EMI irradiations under control.

Figure 9. di/dt vs. gate resistance value @ total parasitic inductance of 110 nH on the power loop

 
 


Figure 10. I_{peak} vs. di/dt @ $P_{\text{OUT}} = 1900 \text{ W}$ 


4 SiC technology vs. silicon

When using very fast power MOSFETs, the use of very fast diodes is also necessary in order to prevent failures. Unfortunately, due to the relatively slow recovery of silicon diodes, (even ultra-fast silicon diodes) they cannot be used in this project. In order to meet the new requirements, ST has developed and introduced a new family of diodes using the new silicon carbide technology. Silicon carbide diodes are virtually free of recovery current, even if, due to the charge and discharge of the parasitic capacitance, a peak current is still present during commutation. But this peak value is very low compared to a silicon diode using the same forward and breakdown voltage. These devices are the best choice for a high-end solar application where performance is the primary target. A comparison between SiC and silicon diodes has been performed in a side-by-side test between a silicon ultra-fast diode and a SiC with the same forward parameters, and using a $di/dt = 800 \text{ A}/\mu\text{s}$. [Table 2](#) provides the results of this comparison. [Figure 11](#) shows the recovery at $I_F = 5 \text{ A}$. This clearly shows that the silicon diode has a Q_{rr} that is ten times higher and more than 3 times the I_{RM} of the SiC diodes. This higher peak current triggers an immediate failure of the power MOSFET if it is used on the converter prototype. In other words, silicon diodes cannot be used in this type of design where the di/dt is very high (from $800 \text{ A}/\mu\text{s}$ to $2000 \text{ A}/\mu\text{s}$).

Table 2. Silicon vs. SiC diode comparison @ $I_F = 5 \text{ A}$, $di/dt = 840 \text{ A}/\mu\text{s}$

Parameter	STPCS1006D	STTH8L06D
$V_F @ 5 \text{ A}, T_J = 25^\circ\text{C}$	1.12	1.2
$V_F @ 5 \text{ A}, T_J = 150^\circ\text{C}$	1.12	0.9
$Q_{rr} \text{ (nC)}$	26	293
$I_{RM} \text{ (A)}$	3.7	9.9
$T_{rr} \text{ (ns)}$	13	44

Figure 11. Silicon vs. SiC diode comparison @ $I_F = 5 \text{ A}$, $di/dt = 840 \text{ A}/\mu\text{s}$

 

5 Conclusion

The special requirements of the photovoltaic field provide an interesting application area for ST's new MDmesh™ V power MOSFETs and SiC diodes. These new technologies can operate at high frequencies with very good efficiency, leading to a reduction in the size of passive components, saving cost and board space. These innovative devices are tested in a new PV inverter prototype. Thanks to performance of the 600-650 V power MOSFETs and diodes used in the prototype, a new inverter topology is possible which permits galvanic insulation with a good trade-off between cost, weight and size.

6 Revision history

Table 3. Document revision history

Date	Revision	Changes
14-May-2010	1	Initial release.

Please Read Carefully:

Information in this document is provided solely in connection with ST products. STMicroelectronics NV and its subsidiaries ("ST") reserve the right to make changes, corrections, modifications or improvements, to this document, and the products and services described herein at any time, without notice.

All ST products are sold pursuant to ST's terms and conditions of sale.

Purchasers are solely responsible for the choice, selection and use of the ST products and services described herein, and ST assumes no liability whatsoever relating to the choice, selection or use of the ST products and services described herein.

No license, express or implied, by estoppel or otherwise, to any intellectual property rights is granted under this document. If any part of this document refers to any third party products or services it shall not be deemed a license grant by ST for the use of such third party products or services, or any intellectual property contained therein or considered as a warranty covering the use in any manner whatsoever of such third party products or services or any intellectual property contained therein.

UNLESS OTHERWISE SET FORTH IN ST'S TERMS AND CONDITIONS OF SALE ST DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY WITH RESPECT TO THE USE AND/OR SALE OF ST PRODUCTS INCLUDING WITHOUT LIMITATION IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE (AND THEIR EQUIVALENTS UNDER THE LAWS OF ANY JURISDICTION), OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.

UNLESS EXPRESSLY APPROVED IN WRITING BY AN AUTHORIZED ST REPRESENTATIVE, ST PRODUCTS ARE NOT RECOMMENDED, AUTHORIZED OR WARRANTED FOR USE IN MILITARY, AIR CRAFT, SPACE, LIFE SAVING, OR LIFE SUSTAINING APPLICATIONS, NOR IN PRODUCTS OR SYSTEMS WHERE FAILURE OR MALFUNCTION MAY RESULT IN PERSONAL INJURY, DEATH, OR SEVERE PROPERTY OR ENVIRONMENTAL DAMAGE. ST PRODUCTS WHICH ARE NOT SPECIFIED AS "AUTOMOTIVE GRADE" MAY ONLY BE USED IN AUTOMOTIVE APPLICATIONS AT USER'S OWN RISK.

Resale of ST products with provisions different from the statements and/or technical features set forth in this document shall immediately void any warranty granted by ST for the ST product or service described herein and shall not create or extend in any manner whatsoever, any liability of ST.

ST and the ST logo are trademarks or registered trademarks of ST in various countries.

Information in this document supersedes and replaces all information previously supplied.

The ST logo is a registered trademark of STMicroelectronics. All other names are the property of their respective owners.

© 2010 STMicroelectronics - All rights reserved

STMicroelectronics group of companies

Australia - Belgium - Brazil - Canada - China - Czech Republic - Finland - France - Germany - Hong Kong - India - Israel - Italy - Japan - Malaysia - Malta - Morocco - Philippines - Singapore - Spain - Sweden - Switzerland - United Kingdom - United States of America

www.st.com

